



modelling "trickier" functions

finite difference method

numerically modeling a low pass circuit

Current :

Current ~~is~~ ^{through} resistor (I_1) = $\frac{V_{in} - V_{out}}{R}$

Must be the same at all points series

Current through capacitor (I_2) = $\frac{dQ}{dt} = C \frac{dV}{dt}$

low-pass cut-off frequency = $\frac{1}{2\pi RC}$

above: $V_{in} = V_{out}$

below: V_{out} is attenuated and phase-shifted

$\therefore \frac{V_{in} - V_{out}}{R} = C \frac{dV}{dt}$

Somehow solved analytically

$V_{out} = V_{in} + Ae^{-t/RC}$

this is one way to solve it but modeling is apparently easier.

Finite difference method

a way of doing a derivative with a computer, producing an estimate

* $\frac{dV}{dt} = \lim_{\Delta t \rightarrow 0} \left[\frac{V(t) - V(t - \Delta t)}{\Delta t} \right]$

$\frac{V_{in}(t) - V_{out}(t)}{R} = C \frac{V_{out}(t) - V_{out}(t - \Delta t)}{\Delta t}$

Solving for $V_{out}(t)$: $V_{out}(t) = V_{in}(t) + \frac{RC}{\Delta t} (V_{out}(t - \Delta t))$

Sine wave Square wave etc

what do I expect for this based on my V_{in}

$\frac{RC}{\Delta t} + 1$

Sine Wave: V_{max} Phase Freq

$V = V_{max} \sin(\omega t + \phi)$

V_{out} simulation using V_{in} as Sine wave

- ① Pick $R, C, \Delta t$
- ② get t data points
- ③ get V_{in} data points
- ④ plot and adjust R, C and Δt to make it "siney"
- ⑤ get V_{out} data points
- ⑥ plot V_{out}

